

Logical Circuit & Design Homework #02			
Due date	May 11, 2020	Instructor	Yoo, Younghwan
Student ID	201445825	Name	이승엽

1. A majority function has an output value of 1 if there are more 1s than 0s on its inputs. The output is 0 otherwise. Design a four-input majority function.

A	B	C	D	out
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

1s > 0s \Rightarrow 1
 0s \geq 1s \Rightarrow 0

CD	00	01	11	10
AB				
00				
01			1	
11		1	1	1
10		1	1	1

$$\Rightarrow f = BCD + ABD + ABC + ACD$$

2. Design a circuit with a 3-bit input A, B, and C, in the form of Gray code, that produces a 3-bit output X, Y, and Z in binary form. For example, if the Gray code inputs are 001 and 011, then the circuit will produce 001 and 010, respectively.


A	B	C	X	Y	Z
0	0	0	0	0	0
0	0	1	0	0	1
0	1	1	0	1	0
0	1	0	0	1	1
1	1	0	1	0	0
1	1	1	1	0	1
1	0	1	1	1	0
1	0	0	1	1	1

\Rightarrow


$$X = A$$

$$Y = A \oplus B$$


$$Z = A \oplus B \oplus C$$

 

 3. Perform technology mapping to NAND gates for the circuit in the following figure. Use cell types selected from: Inverter (n=1), 2NAND, 3NAND, and 4NAND, as defined at the beginning of Section 3-2.



 NAND 게이트는 $\neg(A \cdot B)$, $\neg A$, $\neg B$, $A \vee B$ 를 표현 가능하다.



4. A combinational circuit is defined by the following three Boolean functions:

$$F_1 = \overline{X}Y\overline{Z} + \overline{X}\overline{Y}Z + X\overline{Y}\overline{Z}$$

$$F_2 = \overline{X}YZ + YZ$$

$$F_3 = YZ + XY$$

$$F_4 = \overline{X}Y + XY\overline{Z}$$


Design the circuit with a decoder and external OR gates.

$$F_1 = \overline{X}Y\overline{Z} + \overline{X}\overline{Y}Z + X\overline{Y}\overline{Z} = \sum(1, 2, 4)$$

$$F_2 = \overline{X}YZ + (X + \overline{X})YZ = \overline{X}YZ + X\overline{Y}Z + \overline{X}\overline{Y}Z = \sum(0, 3, 7)$$

$$F_3 = (X + \overline{X})YZ + XY(Z + \overline{Z}) = X\overline{Y}Z + \overline{X}\overline{Y}Z + X\overline{Y}\overline{Z} + X\overline{Y}Z = \sum(3, 6, 7)$$
 
$$F_4 = \overline{X}Y(Z + \overline{Z}) + XY\overline{Z} = \overline{X}YZ + \overline{X}\overline{Y}\overline{Z} = \sum(2, 3)$$



5. Perform the indicated subtractions with the following unsigned binary numbers by taking the 2's complement of the subtrahend:

(a) $11010 - 10001$

(b) $11110 - 1110$

(c) $101001 - 101$

(a) $11010 - 10001 \Rightarrow 10001 = 01111$ (2's complement).

$$\Rightarrow \begin{array}{r} 11010 \\ + 01111 \\ \hline 101001 \end{array} \Rightarrow 01001$$

(b) $11110 - 1110 \Rightarrow 11110 + 0010 = 00000$ (2).

$$\Rightarrow \begin{array}{r} 11110 \\ + 0010 \\ \hline 100000 \end{array}$$

(c) $101001 - 101 = 101001 + 011 \Rightarrow \begin{array}{r} 101001 \\ + 011 \\ \hline 101100 \end{array} \Rightarrow \text{사칙수 증가}$

$$\Rightarrow 010100 \Rightarrow -010100$$

6. Use contraction beginning with a 4-bit adder with carry out to design (a 4-bit increment circuit) with carry out that is incremented by 0011. The function to be implemented is $S = A + 0011$. Design the circuit with AND-OR-XOR gates.

Input				Output			
a_3	a_2	a_1	a_0	S_3	S_2	S_1	S_0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	1	1	0	1
1	0	1	1	1	1	1	0
1	1	0	0	1	1	1	1
1	1	0	1	0	0	0	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	1	0

$$S_3 \Rightarrow \begin{array}{c|cccc} a_3 a_2 & 00 & 01 & 11 & 10 \\ \hline 00 & 0 & 0 & 0 & 0 \\ 01 & 0 & 1 & 1 & 1 \\ 11 & 1 & 0 & 0 & 0 \\ 10 & 1 & 1 & 1 & 1 \end{array}$$

$$= \bar{a}_2 a_3 + \bar{a}_0 \bar{a}_2 a_3 + a_0 a_2 \bar{a}_3 + a_2 \bar{a}_3$$

$$S_2 \Rightarrow \begin{array}{c|cccc} a_3 a_2 & 00 & 01 & 11 & 10 \\ \hline 00 & 0 & 1 & 1 & 1 \\ 01 & 1 & 0 & 0 & 0 \\ 11 & 1 & 0 & 0 & 0 \\ 10 & 0 & 1 & 1 & 1 \end{array}$$

$$= \bar{a}_0 \bar{a}_1 a_2 + a_0 \bar{a}_2 + \bar{a}_0 a_1 \bar{a}_2 = \bar{a}_0 (a_1 \oplus a_2) + a_0 \bar{a}_2$$

$$S_1 \Rightarrow \begin{array}{c|cccc} a_3 a_2 & 00 & 01 & 11 & 10 \\ \hline 00 & 1 & 0 & 1 & 0 \\ 01 & 1 & 0 & 1 & 0 \\ 11 & 1 & 0 & 1 & 0 \\ 10 & 1 & 0 & 1 & 0 \end{array}$$

$$= \bar{a}_0 \bar{a}_1 + a_0 a_1 = (a_0 \oplus a_1) = (a_0 \oplus a_1) \oplus 1$$

$$S_0 \Rightarrow \begin{array}{c|cccc} a_3 a_2 & 00 & 01 & 11 & 10 \\ \hline 00 & 1 & 0 & 0 & 1 \\ 01 & 1 & 0 & 0 & 1 \\ 11 & 1 & 0 & 0 & 1 \\ 10 & 1 & 0 & 0 & 1 \end{array}$$

$$= \bar{a}_0 \bar{a}_1 + \bar{a}_0 a_1 = \bar{a}_0 = a_0 \oplus 1$$

